

**San Jose State University**  
**Department of Computer Engineering**

## **CMPE 200 Report**

---

### **Assignment 5 Report**

**Title** Processor Design (1): Design Code Review and Functional Verification

**Semester** Fall 2022

**Date** 10/10/2022

**by**

**Name** Tirumala Saiteja Goruganthu  
*(typed)*

**SID** 016707210  
*(typed)*

## **ABOUT THE AUTHOR**

I am Saiteja and I am from Hyderabad, India. I completed my bachelors in Electronics and Communication Engineering from Gokaraju Rangaraju Institute of Engineering and Technology with a CGPA of 9.97/10 in the year 2019. I received a Gold Medal for the academic excellence from my university. Right after that, I got an opportunity to work for Tata Consultancy Services as a Systems Engineer and have worked for 3 years until July 2022. I speak English, Hindi, and Telugu where the last of these is my first language. My interests include but not limited to Cricket, Table-Tennis and learning new languages. Currently I am pursuing my master's in Computer Engineering at San Jose State University.

## TABLE OF CONTENTS

<b><i>LIST OF FIGURES \ TABLES.....</i></b>	<b><i>3</i></b>
<b><i>INTRODUCTION:.....</i></b>	<b><i>4</i></b>
<b><i>MY GROUP: .....</i></b>	<b><i>4</i></b>
<b><i>GIVEN TASK:.....</i></b>	<b><i>4</i></b>
<b><i>STEPS TAKEN TO COMPLETE THE TASK:.....</i></b>	<b><i>4</i></b>
<b><i>DISCUSSION SECTION:.....</i></b>	<b><i>5</i></b>
1) Datapath Explanation: .....	5
2) Control Path Explanation: .....	9
3) Memory Explanation: .....	11
4) Processor Core Explanation: .....	12
5) Complete Processor Explanation: .....	12
6) Simulating in Vivado: .....	13
<b><i>COLLABORATION SECTION: .....</i></b>	<b><i>14</i></b>
<b><i>CONCLUSION: .....</i></b>	<b><i>14</i></b>
<b><i>APPENDIX .....</i></b>	<b><i>15</i></b>
1) Block Diagram of the Single-Cycle MIPS Datapath.....	15
2) Block Diagram of the Single-Cycle MIPS Controlpath.....	16
3) Block Diagram of the Instruction Memory .....	16
4) Block Diagram of the Data Memory .....	16
5) Block Diagram of the Processor-Core.....	17
6) Block Diagram of the Complete Processor .....	17
7) Output Waveforms After the Simulation .....	18

## **LIST OF FIGURES \ TABLES**

Table5.1 – Signal-Description table for the D-Register

Table5.2 – Signal-Description table for the 32-bit adder

Table5.3 – Signal-Description table for the 2x1 multiplexer

Table5.4 – Signal-Description table for the Sign Extension Unit

Table5.5 – Signal-Description table for the Register File

Table5.6 – Signal-Description table for the ALU

Table5.7 – Truth-Table observed in alu.v file

Table5.8 – Signal-Description table for the Datapath

Figure5.9 – Datapath of the Single-Cycle MIPS Processor

Table5.10 – Signal-Description table for the Main Decoder

Table5.11 – Signal-Description table for the Auxiliary Decoder

Figure5.12 – Control Unit of the Single-cycle MIPS Processor

Figure5.13 – Block Diagram of the Instruction Memory

Figure5.14 – Block Diagram of the Data Memory

Figure5.15 – Block Diagram of the Processor Core

Figure5.16 – Block Diagram of the Complete Processor

Figure5.17 – Waveform after verifying the Single-cycle MIPS Processor Functionality.

Figure5.18 – Waveform after verifying the Single-cycle MIPS Processor Functionality.

## INTRODUCTION:

This activity is to gain hands-on processor design experience by reviewing RTL Verilog design code for the initial version of the single-cycle MIPS processor discussed in class. Apart from that, we learn the basic technique for functionally verifying a processor.

## MY GROUP:

**Name:** Student\_Team 6

**Members:** Tirumala Saiteja Goruganthu (016707210), Harish Marepalli (016707314)

## GIVEN TASK:

The task is to carefully study the source code you obtained from the archive, then based on the source, draw the block diagrams of the following, for the initial design of the MIPS processor:

- a) Datapath with microarchitecture details (not including memories).
- b) Control unit with microarchitecture details.
- c) Instruction memory and data memory.
- d) Processor core (show interconnection between the datapath and its control unit, datapath internal microarchitecture is not required).
- e) Complete processor (show interconnections between the processor core and its memories).

Another task is to use the resources included in the archive, build the DUT (the initial design of the single-cycle MIPS) and its test bench, then functionally verifying the MIPS processor based on the given sample program.

## STEPS TAKEN TO COMPLETE THE TASK:

- a. Spent time to understand the question carefully.
- b. Noted down all the high level as well as low level datapath, controlpath, instruction memory, data memory, processor core, complete processor signals using the Verilog code given in the archive.
- c. Drawn the datapath block diagram with the above notes and using Visio to build the building blocks.
- d. Similarly drawn the controlpath, instruction memory, data memory, processor core, complete processor block diagrams with the above notes and using Visio to build the building blocks.
- e. After completing the task1, started creating a new project in Vivado Xilinx tool.
- f. Imported the given sources as well as the simulation testbench from the archive into the project.
- g. Altered the *memfile.dat* location by putting the file in current working directory. This file is important since it has all the instruction machine codes that are needed for execution.
- h. After the project setup is done, clicked on “*Run Simulation*” button to execute the test bench.
- i. Finally, output waveforms are simulated and observed in the Vivado tool.

## DISCUSSION SECTION:

### 1) Datapath Explanation:

From the Verilog file “*datapath.v*”, we can observe that six leaf-level modules are used to instantiate the whole datapath (albeit some modules may be used multiple times). In this section, we will try to visually (in the form of tables) show the input-output structure of each leaf-level module and then we traverse our way back up to the datapath module.

- a. The D-Register module named “*dreg*” contains three inputs and one output. The main logic here is that for every positive clock edge and positive reset edge we will start the execution. If the reset (*rst*) signal is asserted, then assign logic ‘0’ to the output (*q*), else assign the input (*d*) to the output (*q*). The following table (*Table5.1*) will illustrate the Signal-Description relationship.

Signal Name	Description (Input / Output)
clk	Clock signal (Input)
rst	Reset Signal (Input)
d[31:0]	Input Signal (Input)
q[31:0]	Output Signal (Output)

*Table5.1 – Signal-Description table for the D-Register*

- b. The 32-bit adder module named “*adder*” contains two inputs and one output. The main logic here is written in behavioral way where just a single instruction ( $y = a + b$ ) is enough to realize a 32-bit adder. The following table (*Table5.2*) will illustrate the Signal-Description relationship.

Signal Name	Description (Input / Output)
a[31:0]	Operand 1 (Input)
b[31:0]	Operand 2 (Input)
y[31:0]	Result (Output)

*Table5.2 – Signal-Description table for the 32-bit adder*

- c. The 2x1 multiplexer module named “*mux2*” contains two inputs, one output and one selection line to select the required input line. The main logic here is written in behavioral way using the ternary operator ( $y = sel ? b : a$ ) is enough to realize a 2x1 multiplexer. The following table (*Table5.3*) will illustrate the Signal-Description relationship.

Signal Name	Description (Input / Output)
a[7:0]	Operand at 0 port (Input)
b[7:0]	Operand at 1 port (Input)
sel	Selection line (Input)
y[7:0]	Output Signal (Output)

*Table5.3 – Signal-Description table for the 2x1 multiplexer*

- d. The sign extension module named “*signext*” contains one input and one output. The main logic here is to get the MSB of the input, duplicate this bit 16 times and append the new 16-bit string to the already existing 16-bit input (*a*) to form a 32-bit number as output (*y*). The following table (*Table5.4*) will illustrate the Signal-Description relationship.

Signal Name	Description (Input / Output)
a[15:0]	16-bit Input (Input)
y[31:0]	32-bit Output (Output)

*Table5.4 – Signal-Description table for the Sign Extension Unit*

- e. The Register file module named “*regfile*” contains seven inputs and three outputs. Each register in this register file can hold 32-bit data. We realize this using a two-dimensional array. Initialize all the register values to zero and initialize “*sp*” value to 32-bit “b’100” value. The main logic here is that for every positive edge of the clock, if write enable signal (*we*) is enabled then write the data (*wd*) into the provided write address (*wa*). After that, output all three read-data ports (*rd1*, *rd2*, *rd3*) by assigning them with the content at addresses (*ra1*, *ra2*, *ra3*). The following table (*Table5.5*) will illustrate the Signal-Description relationship.

Signal Name	Description (Input / Output)
clk	Clock signal (Input)
we	Write Enable (Input)
ra1[4:0]	Read Address 1 (Input)
ra2[4:0]	Read Address 2 (Input)
ra3[4:0]	Read Address 3 (Input)
wa[4:0]	Write Address (Input)
wd[31:0]	Write Data (Input)
rd1[31:0]	Read Data 1 (Input)
rd2[31:0]	Read Data 2 (Input)
rd3[31:0]	Read Data 3 (Input)

*Table5.5 – Signal-Description table for the Register File*

- f. The Arithmetic and Logical Unit (ALU) module named “*alu*” has three inputs and two outputs. The main logic here is that depending on the “*op*” value, the operation is determined. So, we use switch case to realize the ALU. Apart from that, a “*zero*” flag is set as output to the ALU which will be de-asserted only if the ALU result is logic low. The following table (*Table5.6*) will illustrate the Signal-Description relationship.

Signal Name	Description (Input / Output)
a[31:0]	Operand 1 (Input)
b[31:0]	Operand 2 (Input)
op[2:0]	Operation Select (Input)
zero	Zero Flag (Output)
y[31:0]	Result (Output)

*Table5.6 – Signal-Description table for the ALU*

The following Truth-Table (*Table5.7*) observed from the given Verilog code is as follows:

op value	Corresponding Operation
000	AND
001	OR
010	ADD
110	SUB
111	SLT

*Table5.7 – Truth-Table observed in alu.v file*

- g. Finally, the whole datapath is realized in a module named “*datapath.v*.” We use one or more of the leaf-level to achieve the required datapath. The following table (*Table5.8*) will illustrate the Signal-Description relationship.

The D-Register (*pc\_reg*) is used to store the program counter value with every positive edge of the clock cycle.

The adder (*pc\_plus\_4*) is used to add number 4 to the current program counter to point to the next instruction.

The adder (*pc\_plus\_br*) is used to add *pc\_plus\_4* and the branch address (calculated by multiplying the *signImm* value with 4).

The multiplexer (*pc\_src\_mux*) is used to select either next instruction program counter or the new branch target address.



The multiplexer (*pc\_jump\_mux*) is used to select either next instruction program counter or the new jump target address.

The multiplexer (*rf\_wa\_mux*) is used to select either the  $R_d$  destination register or  $R_t$  destination register depending on the type of instruction.

The Register File (*rf*) is used to as a 32 32-bit register container used for processor operations.

The Sign Extension Unit (*se*) is used to extend the 16-bit input using the MSB and replicating the MSB 16 more times before appending to the original 16-bit input to form a 32-bit output.

The multiplexer (*alu\_pb\_mux*) is used to select either the data from the register file or the sign extension unit depending on the type of instruction.

The Alu (*alu*) is used to perform operations such as add, sub, and, or and slt where these operations are controlled by the  $op[2:0]$  bits.

The multiplexer (*rf\_wd\_mux*) is used to select either the data from the memory or the alu output depending on the type of instruction.

Signal Name	Description (Input / Output)
clk	Clock Signal (Input)
rst	Reset (Input)
branch	Branch Control (Input)
jump	Jump Control (Input)
reg_dst	Destination Register Select (Input)
we_reg	Write Enable for Register File (Input)
alu_src	ALU Source Steering (Input)
dm2reg	Data Memory to RF (Input)
alu_ctrl[2:0]	ALU Control (Input)
ra3[4:0]	Read Address Port 3 (Input)
instr[31:0]	32-bit Instruction (Input)
rd_dm[31:0]	Read data from Data memory (Input)
pc_current[31:0]	Current Program Counter (Output)
alu_out[31:0]	ALU Output (Output)
wd_dm[31:0]	Write data to Data memory (Output)
rd3[31:0]	Read Data Port 3 (Output)

*Table5.8 – Signal-Description table for the Datapath*

Below Figure (Figure 5.9) shows the Datapath Block Diagram for the Single-cycle MIPS CPU.

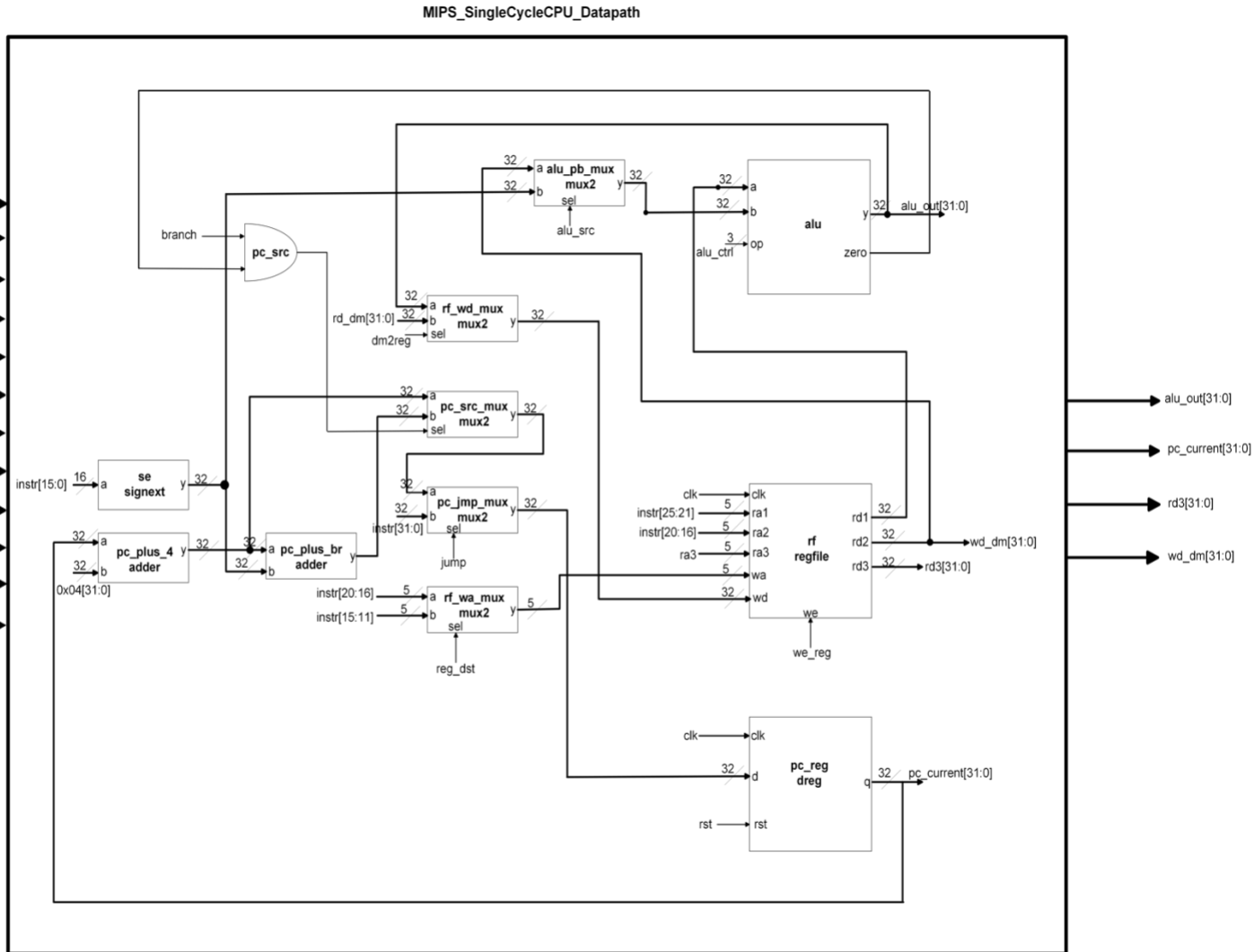


Figure5.9 – Datapath of the Single-Cycle MIPS Processor

## 2) Control Path Explanation:

From the Verilog file “*controlunit.v*”, it is observed that the whole control unit is divided into two categories.

- a. A main decoder to generate all the control signals such as mux selects, branch and jump using the opcode part of the instruction machine code and it also outputs a 2-bit *alu\_op* signal which controls the second *auxiliary* or ALU decoder. Depending upon the opcode bits, the corresponding operation is selected. The following table (Table 5.10) will illustrate the Signal-Description relationship.

Signal Name	Description (Input / Output)
opcode[5:0]	Opcode from the Machine Code (Input)
branch	Branch Control (Output)
jump	Jump Control (Output)
reg_dst	Destination Register Select (Output)
we_reg	Write Enable Register (Output)
alu_src	ALU Source Steering (Output)
we_dm	Write Enable to Data Memory (Output)
dm2reg	Data Memory to RF (Output)
alu_op[1:0]	2-bit ALU Result (Output)


*Table5.10 – Signal-Description table for the Main Decoder*

- b. An Auxiliary or ALU decoder is another module which takes two inputs and sends out one output. Depending on the *funct* field and the *alu\_op* signal, the corresponding operation is realized. If *alu\_op* is either 00 or 01, then the operation is add or subtract, else, the *funct* field is used to realize a particular operation. The following table (Table 5.11) will illustrate the Signal-Description relationship.

Signal Name	Description (Input / Output)
alu_op[1:0]	ALU Input from Main Decoder
funct[5:0]	Function bits from the Machine Code
alu_ctrl[2:0]	ALU Control bits to ALU Module

*Table5.11 – Signal-Description table for the Auxiliary Decoder*

- c. Finally, the whole control unit is designed using the above two modules. The following figure (Figure 5.12) show the control unit block diagram for Single-cycle MIPS CPU.

 


*Figure5.12 – Control Unit of the Single-cycle MIPS Processor*

### 3) Memory Explanation:


By observing the Verilog files related to memory unit, we have two memory partitions. They are instruction memory and data memory.

- a. The instruction memory module named “*imem.v*” consists of one input for 5-bit address and one output for 32-bit data. The instruction memory is realized using a two-dimensional array with 64 rows and 32 columns. A separate “*memfile.dat*” is given in the assignment archive which consists of series of machine codes. When this module is instantiated, the machine codes from this file will be read into the above two-dimensional array. The following figure (*Figure5.13*) shows the block diagram of the instruction memory.

 

*Figure5.13 – Block Diagram of the Instruction Memory*

- b. The data memory module named “*dmem.v*” consists of four inputs and one output. The data memory is realized using a two-dimensional array with 64 rows and 32 columns. When this module is instantiated, all values in the array are initialized to “*FFFFFFFF*.” Now at every positive edge of the clock (*clk*), if the write enable (*we*) signal is asserted, then the data will be written into the array at the given address (*a*). For retrieval purposes, the array will be retrieved with address (*a*) and the corresponding data will be fetched and sent as output (*q*). The following figure (*Figure5.14*) shows the block diagram of the data memory.

 

*Figure5.14 – Block Diagram of the Data Memory*

#### 4) Processor Core Explanation:

By observing the Verilog files for the top-level module for datapath and controlpath, we see that there is another module named “*mips.v*” which instantiates both data and control paths by giving the required signals. It has five inputs and five outputs. The following figure (Figure5.15) shows the block diagram of the Processor Core.

 


Figure5.15 – Block Diagram of the Processor Core

#### 5) Complete Processor Explanation:

The previous Verilog file (*mips.v*) instantiates only datapath and controlpath modules, but the file (*mips\_top.v*) instantiates the *mips.v* module, instruction memory and data memory. The following figure (Figure5.16) shows the block diagram of the Complete Processor.


 



Figure5.16 – Block Diagram of the Complete Processor

## 6) Simulating in Vivado:

A test-bench file has already been given in the assignment archive which has been imported into the simulation sources of the Vivado Xilinx tool. After that, when the “Run Simulation” button is clicked, the waveforms will appear in the tool. The following figures (*Figure5.17* and *Figure5.18*) constitute the waveforms.

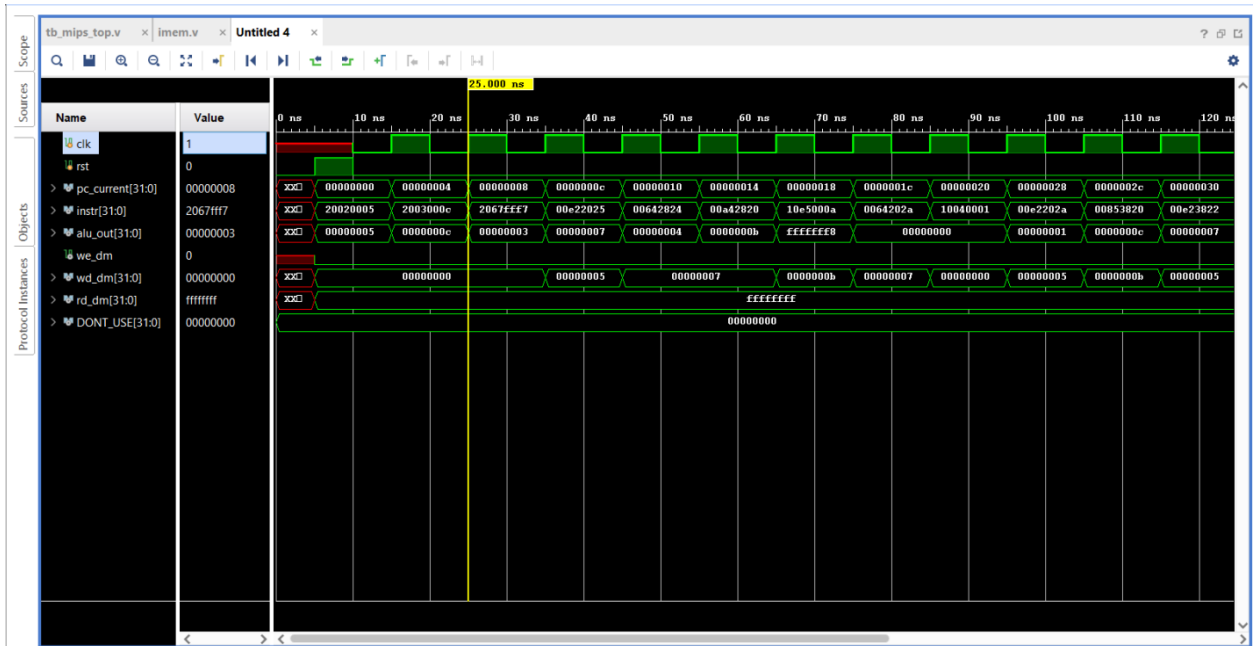

*Figure5.17 – Waveform after verifying the Single-cycle MIPS Processor Functionality.*

 

*Figure5.18 – Waveform after verifying the Single-cycle MIPS Processor Functionality.*

**COLLABORATION SECTION:**


1. Worked together on the datapath and controlpath block diagram designs using Microsoft Visio tool.
2. By collaborating with each other, imported the given source files into Vivado and observed the output waveforms after the simulation.

**CONCLUSION:**

In conclusion, we end the report by understanding the given RTL Verilog code for the initial version of the single-cycle MIPS processor. We also were able to grasp the logic that was written in the Verilog files and along with that we were able to draw block diagrams based on the code. Apart from that, we learnt the basic techniques in functionally verifying a processor.


# APPENDIX
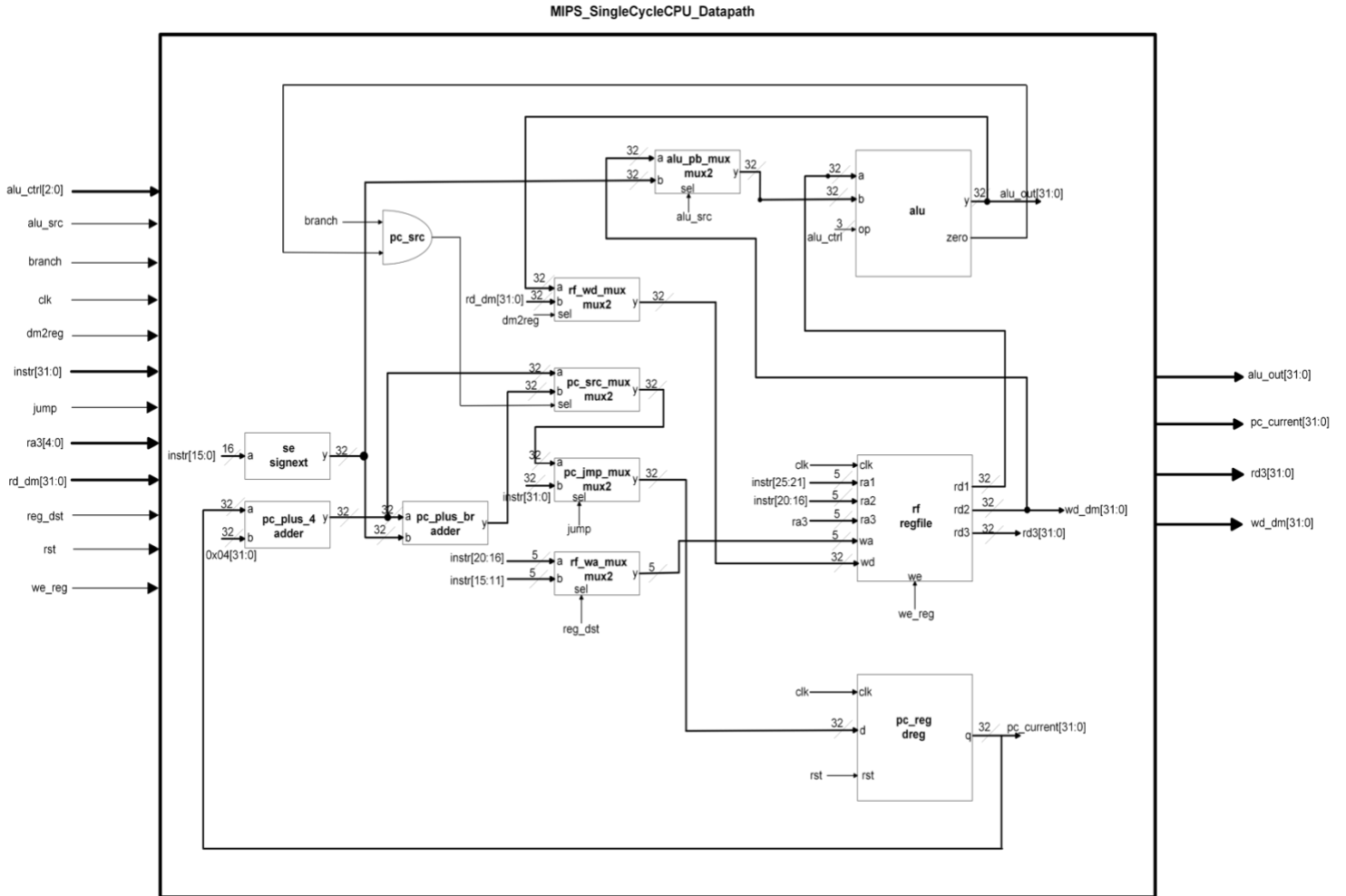
## 1) Block Diagram of the Single-Cycle MIPS Datapath





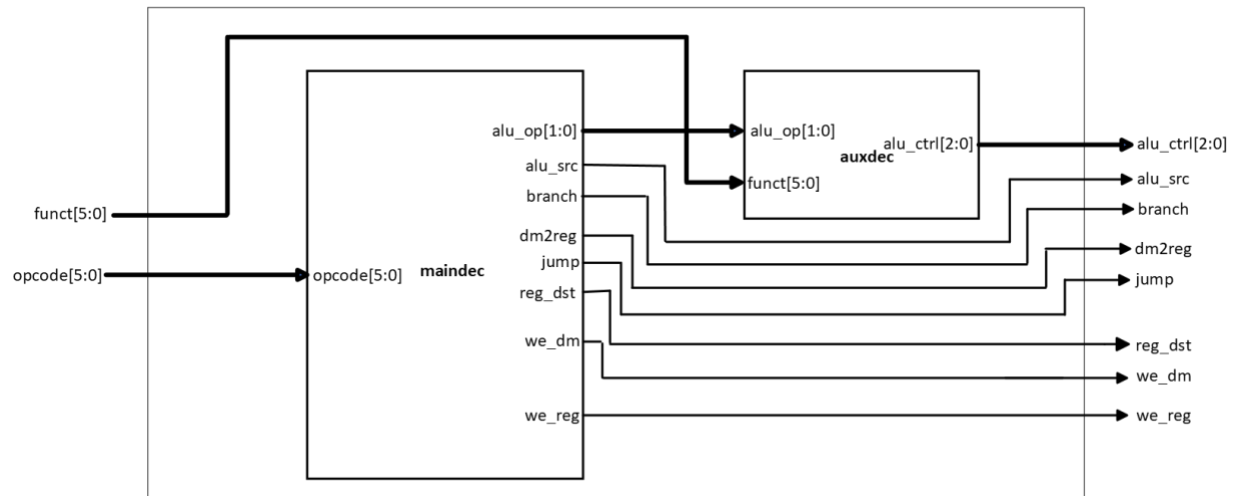
## 2) Block Diagram of the Single-Cycle MIPS Controlpath




## 3) Block Diagram of the Instruction Memory




## 4) Block Diagram of the Data Memory

 
 
## 5) Block Diagram of the Processor-Core


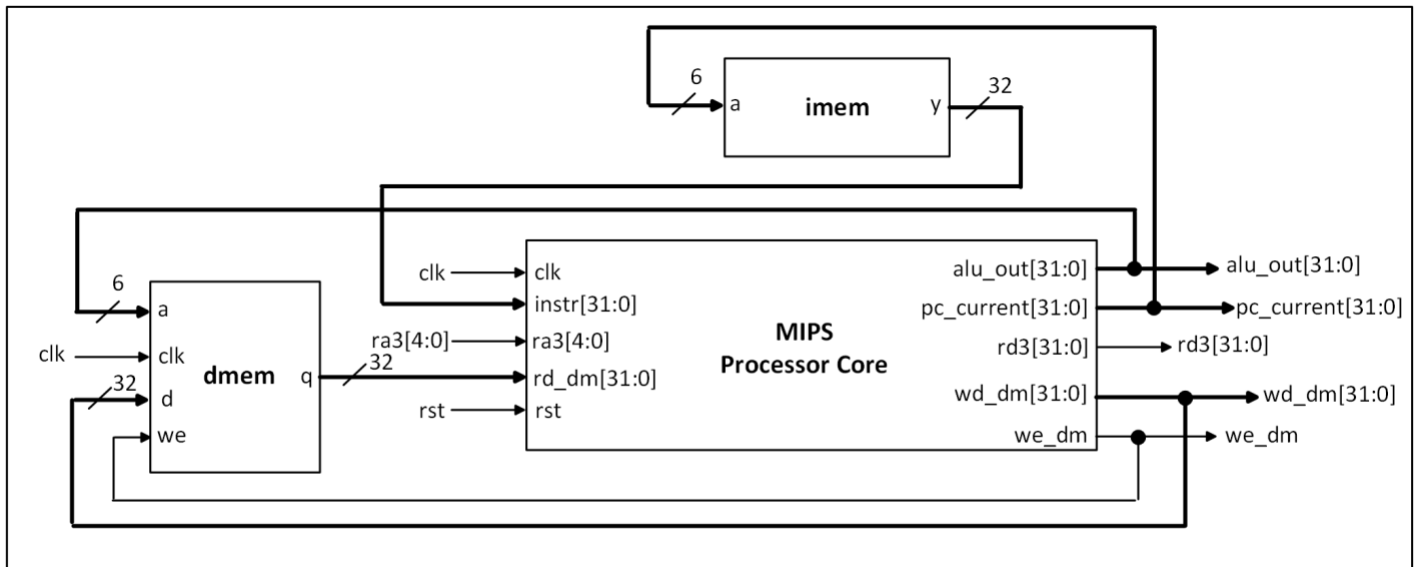
## 6) Block Diagram of the Complete Processor



## 7) Output Waveforms After the Simulation

