

CMPE 200
Computer Architecture & Design


Lecture 3.
Processor Microarchitecture
and Design (1)

Haonan Wang



SAN JOSÉ STATE
UNIVERSITY

Instruction Processing

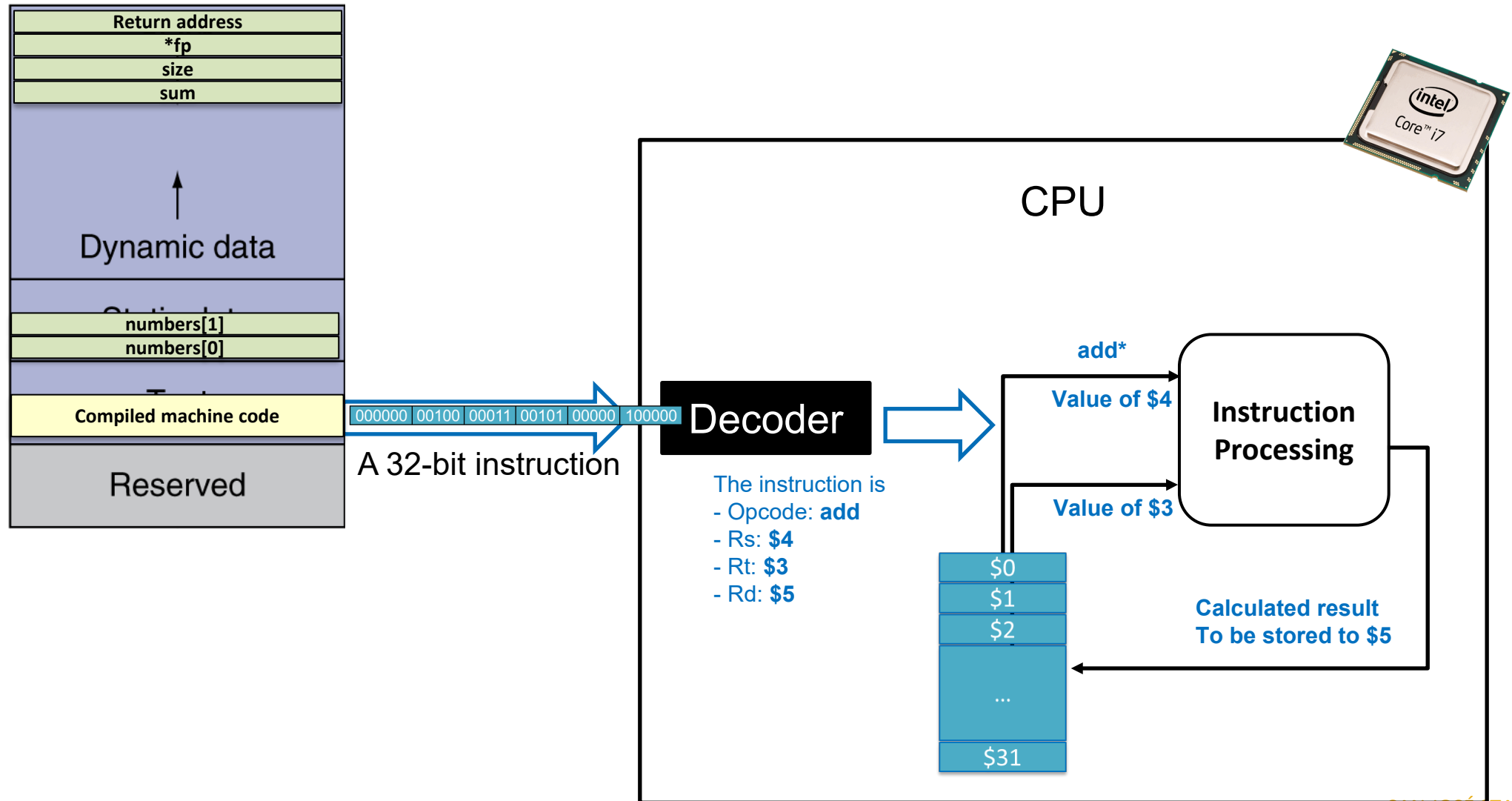

Instruction Execution on CPU

- To run a software, CPU
 - **Fetches** instructions from memory in the right order
 - **Decodes** the instruction and **Reads** the operand values from register file
 - **Executes** the computation by using ALU
 - **Loads/store** data from/to memory
 - **Writes back** the computation results to register file



Implementing a Single-Cycle CPU

- **All instructions execute in a single clock cycle**
 - Instructions to Implement: LW, SW; ADD, SUB, AND, OR, SLT; BEQ
 - CPI = 1
- **Different instructions need different execution times**
 - e.g., LW needs to access memory vs. ADD does not need to access memory
- **Single-cycle CPU's clock cycle period should be set to the **longest instruction's execution time****


Fetch Components

- **Required operations**


- Taking address from PC and reading instruction from memory
- Incrementing PC to point at next instruction

- **Components**

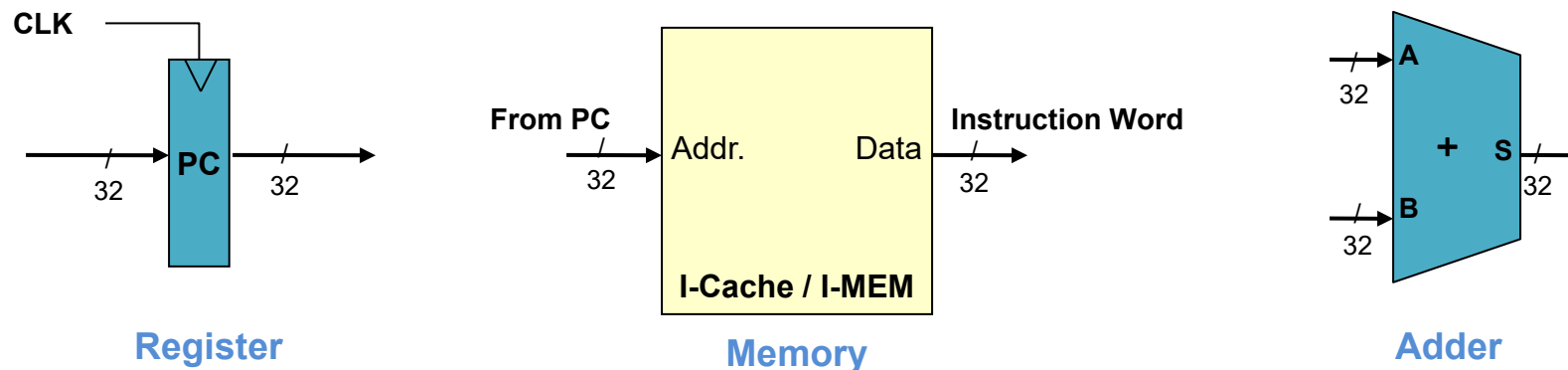- PC register
- Instruction Memory / Cache
- Adder to increment PC value




Fetch Data Path

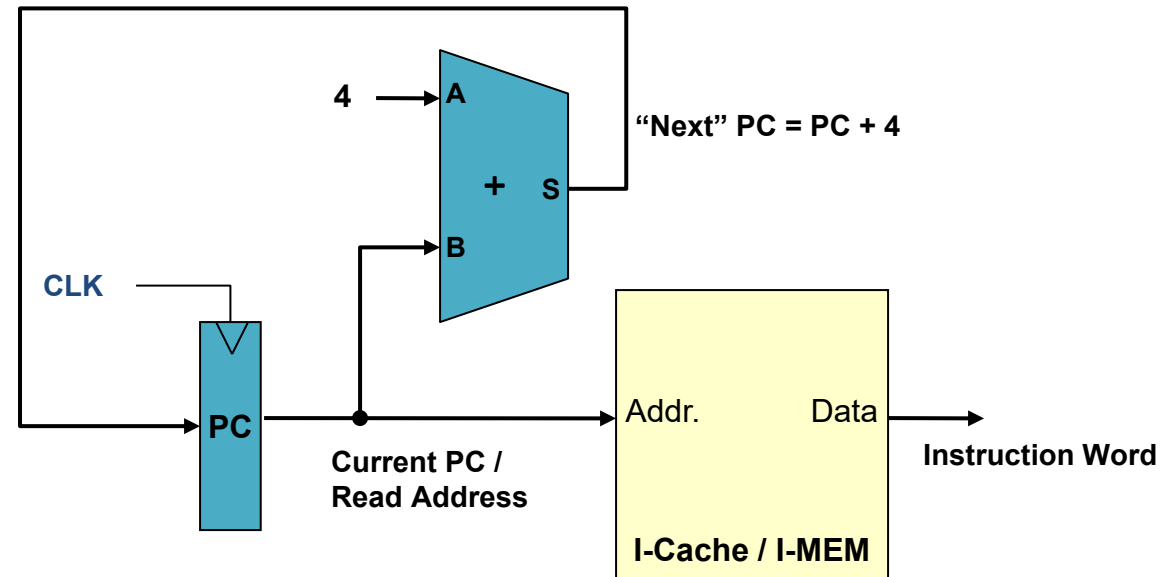


Fetch Data Path

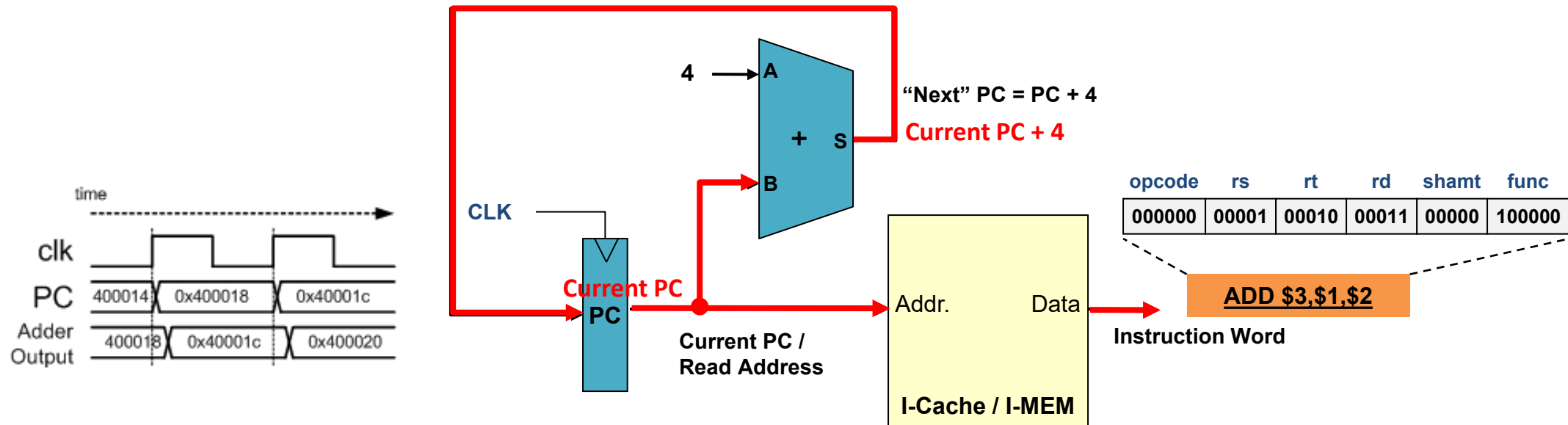- PC value serves as address to instruction memory while also being incremented by 4 using the adder
- Instruction word is returned by memory after some delay
- New PC value is clocked into PC register at the end of clock cycle




Decode

- What is the instruction and operands?

 


Instruction Formats

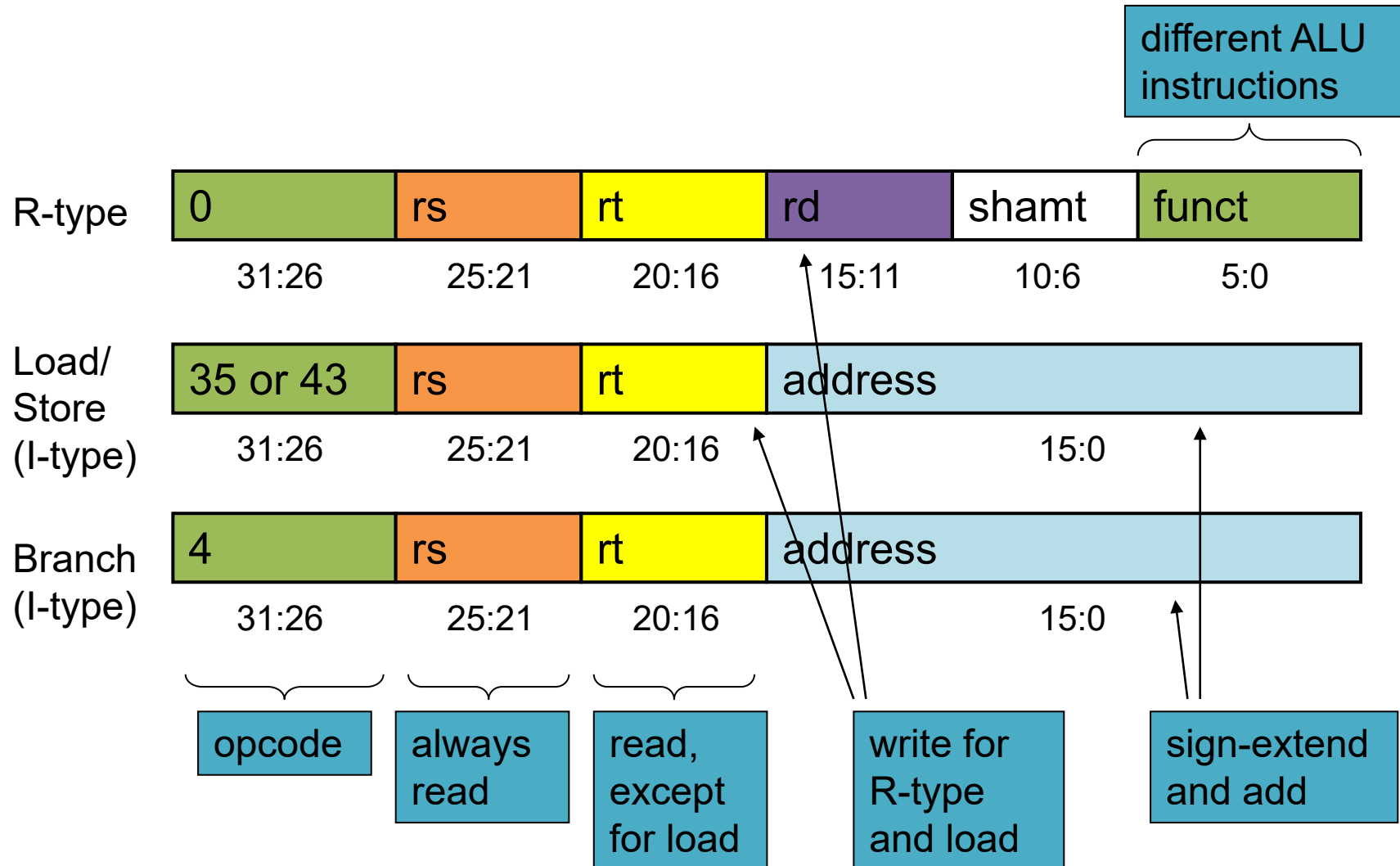

Decode Components

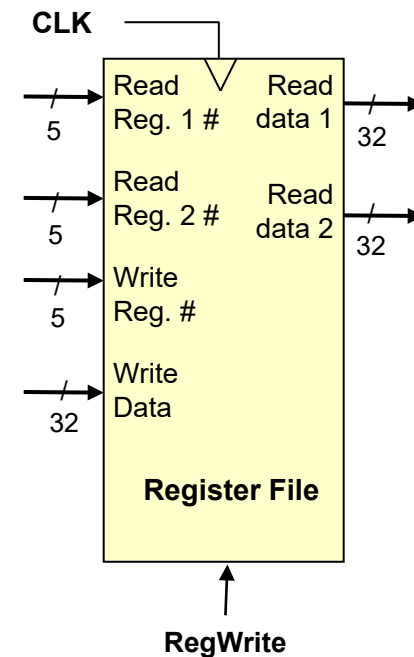
- **Register file is a collection of registers**
- **To support R-type instruction,**
 - 4 Input ports: two src register ids, a dst register id and the result value
 - 2 Output ports: two operand values



Decode Data Path

- **R-type**

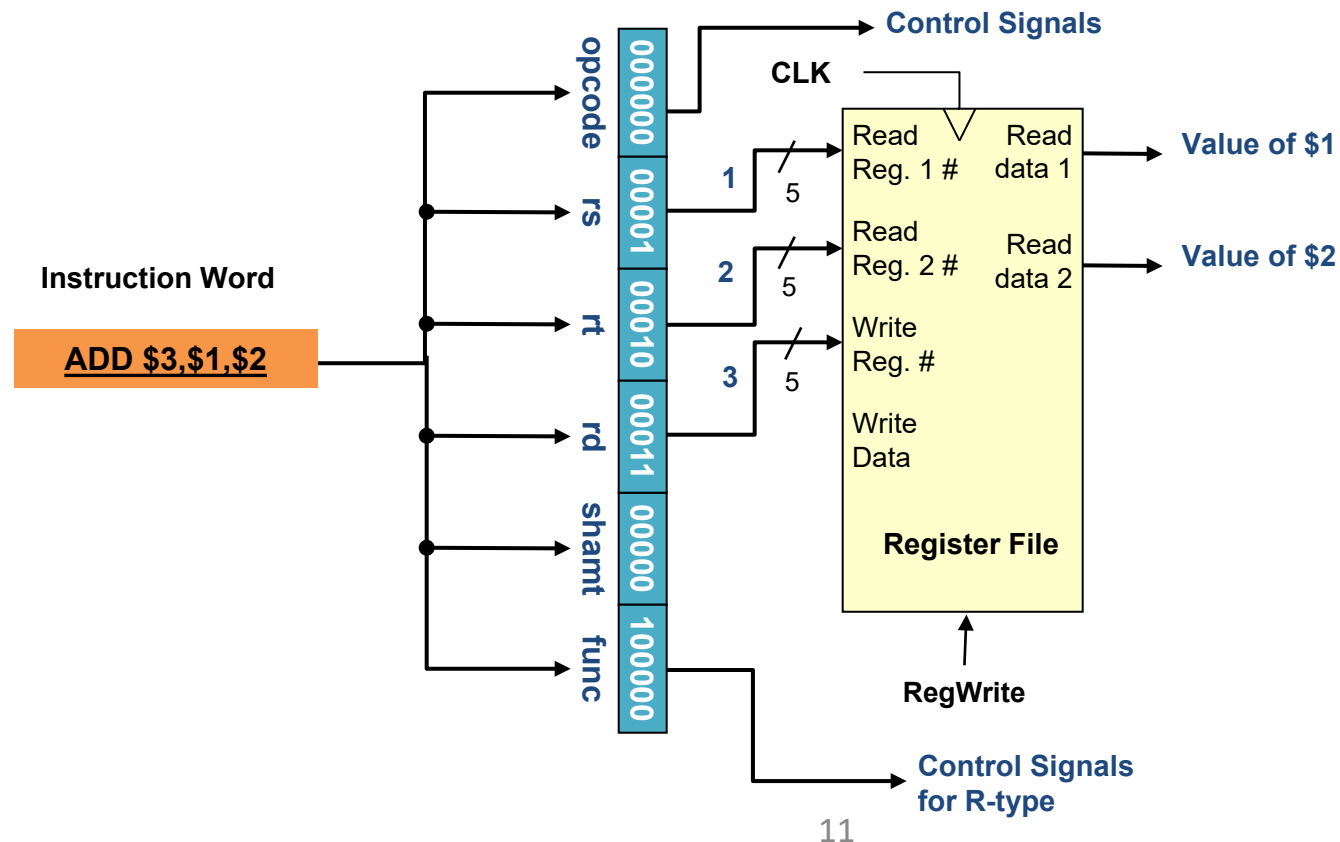- Opcode and func. field are decoded to produce control signals
- Three register ids are passed to Register file



Sign Extension Unit


- In a 'LW' or 'SW' instructions with their base register + offset format, the instruction only contains the offset as a 16-bit value
 - Example: LW \$4,-8(\$1)
 - Machine Code: 0x8c24fff8
- A 16-bit offset must be extended to 32-bits to add to the base register



Decode Data Path


- **I-type**

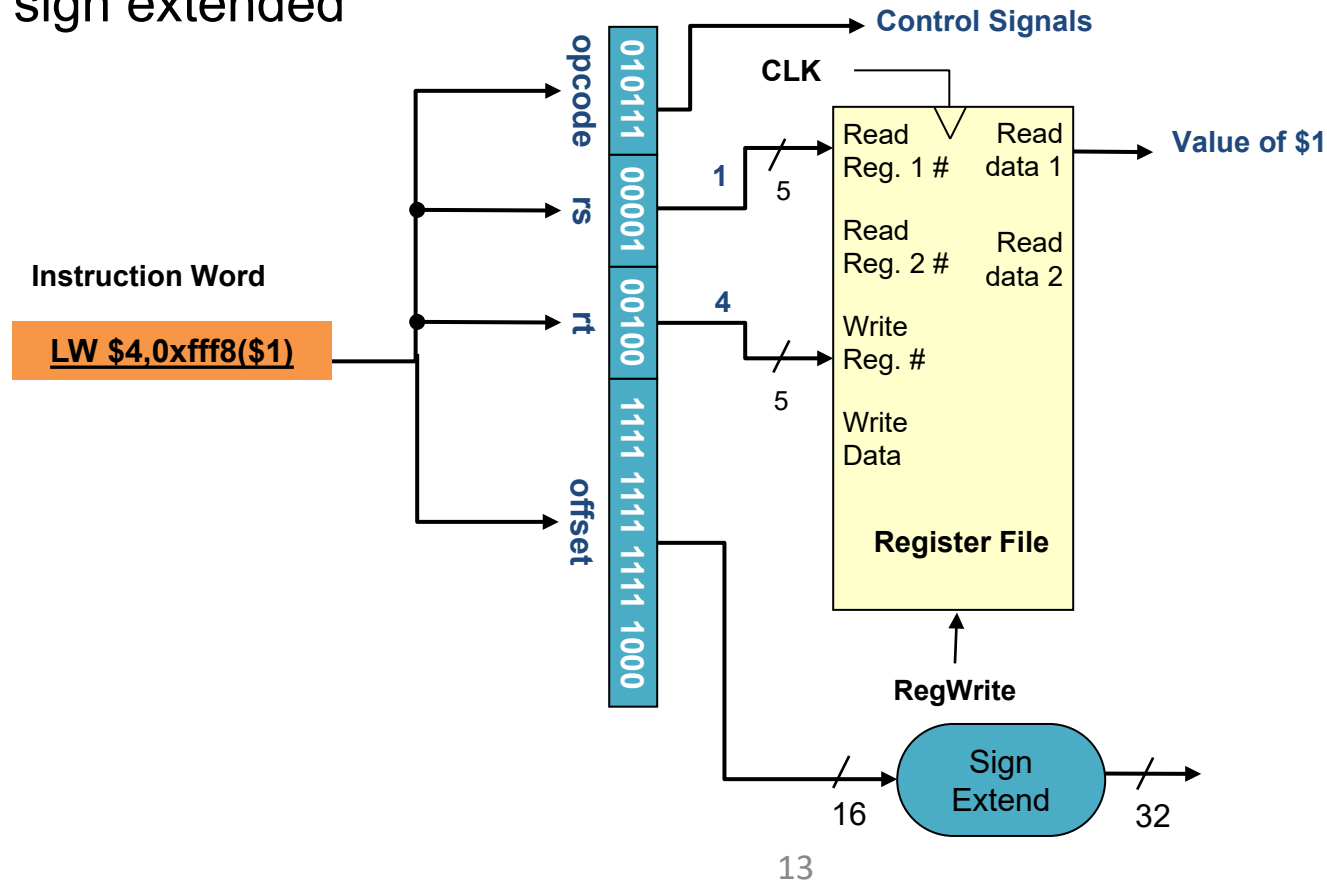- Opcode field is decoded to produce control signals
- Two register ids are passed to Register file
- Offset is sign extended




Execution & Write Result

- Let's execute the instruction!

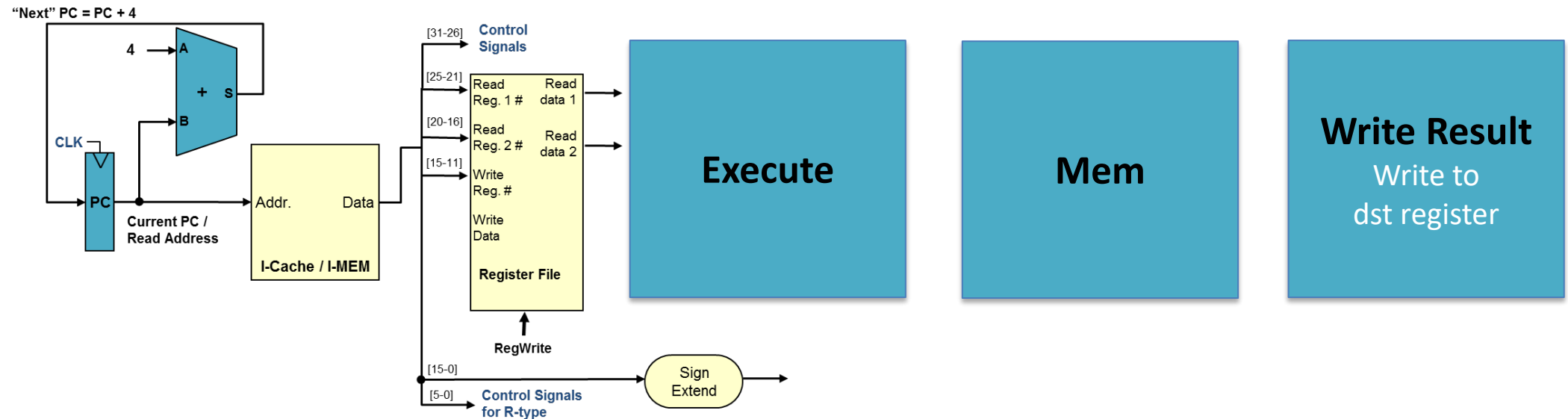


Execution Components

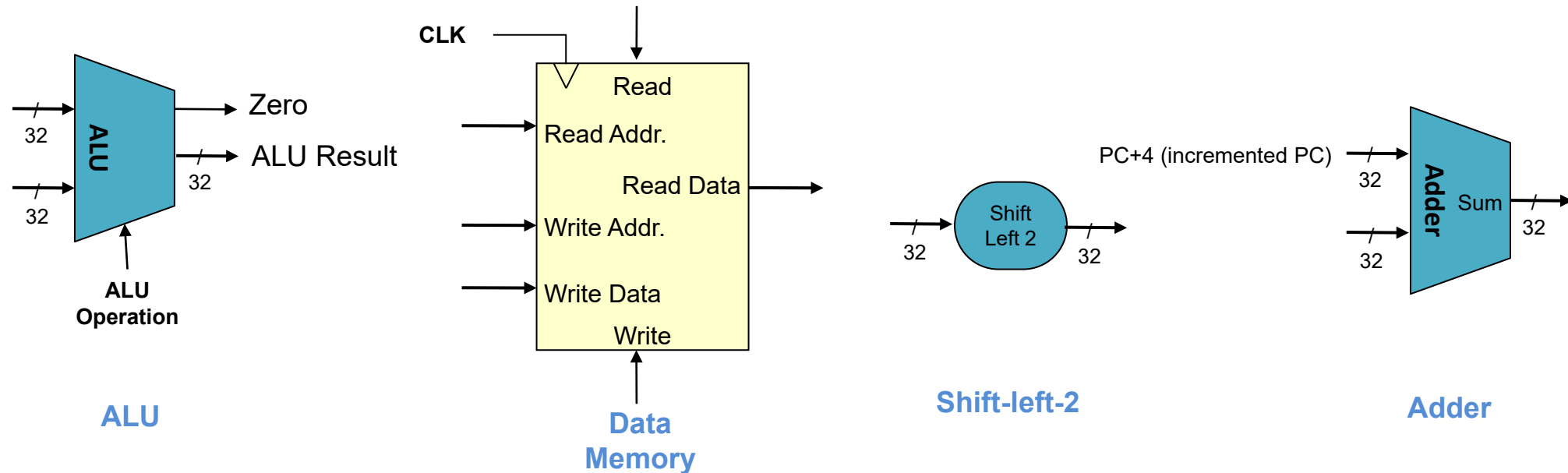- **ALU is used for**
 - R-type instructions to operate various arithmetic operations
 - LW/SW instructions to operate (base address + offset) to generate the target memory address
 - Branch instructions to compare (subtract) the two operand values
- **Data Memory for LW/SW instructions**
- **Shift-left-2 and another Adder for Branch instructions to calculate new PC value**




Datapath for R-type Instructions

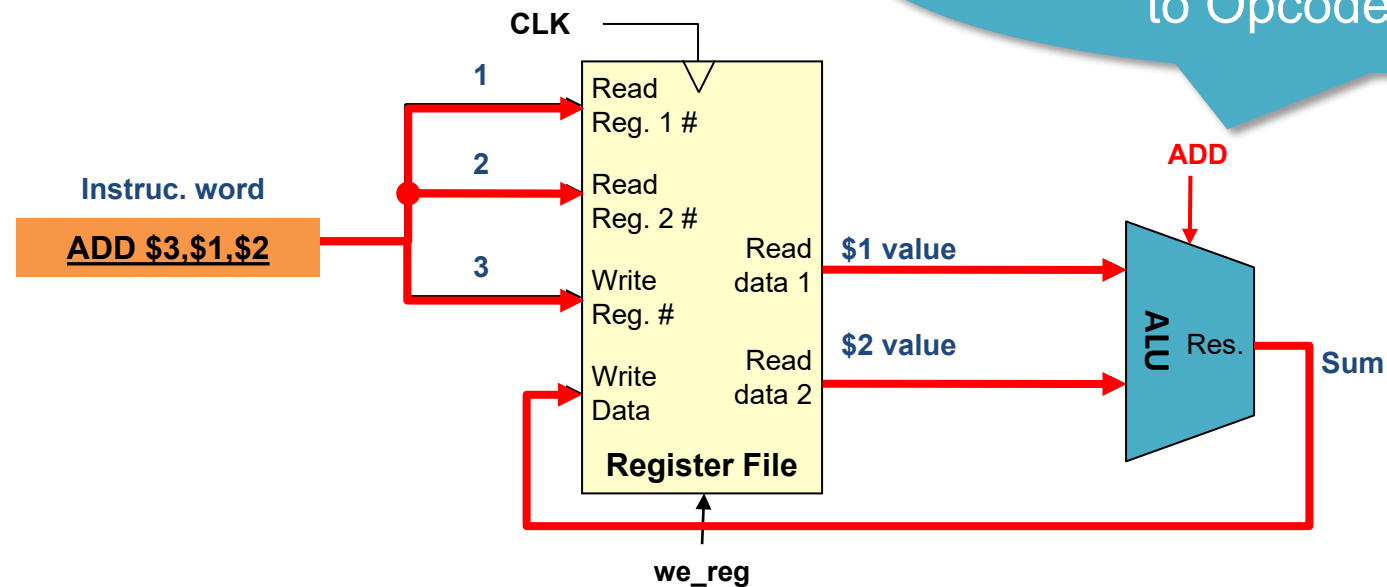- ALU takes inputs from register file and performs the add, sub, and, or, slt, operations
- Result is written back to dest. register




Memory Access Datapath: LW

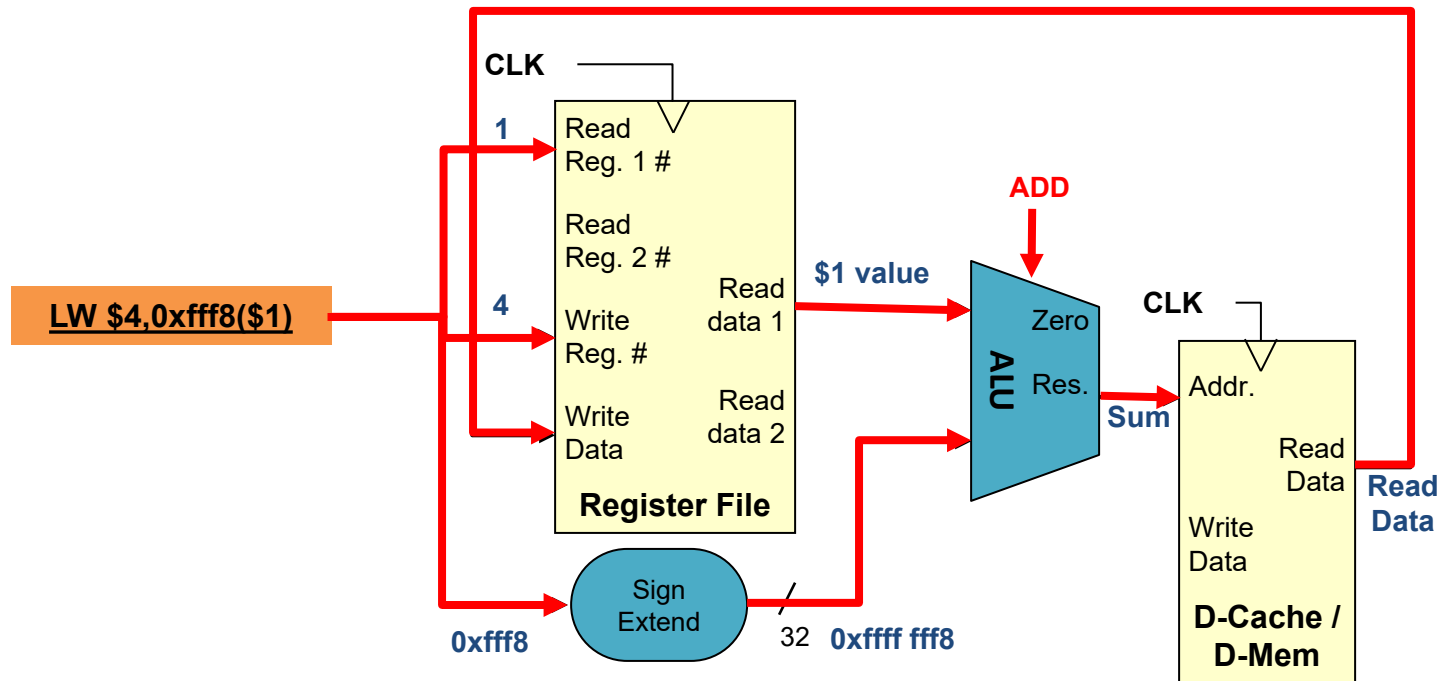- Operands are read from register file while offset is sign extended
- ALU calculates target memory address
- Memory access is performed
- If LW, read data is written back to register




Memory Access Datapath: SW

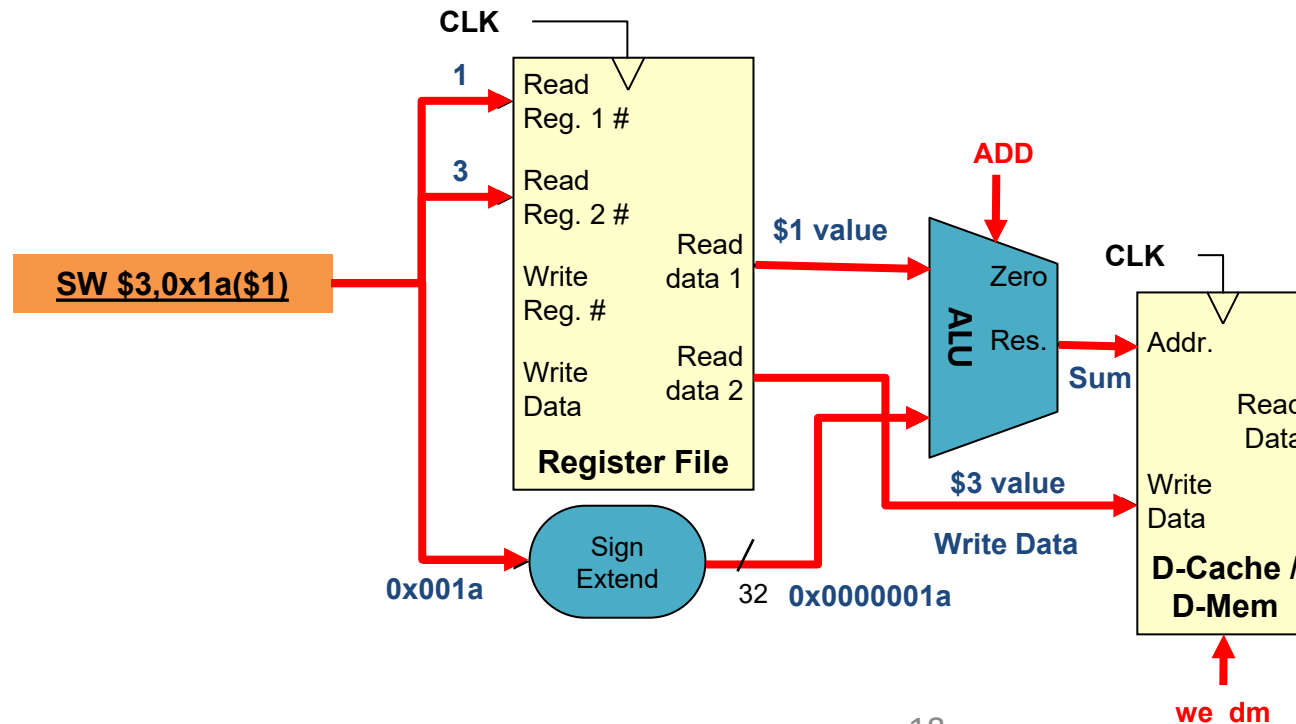- Operands are read from register file while offset is sign extended
- ALU calculates target memory address
- If SW, data is written to the memory



Branch Datapath: BEQ

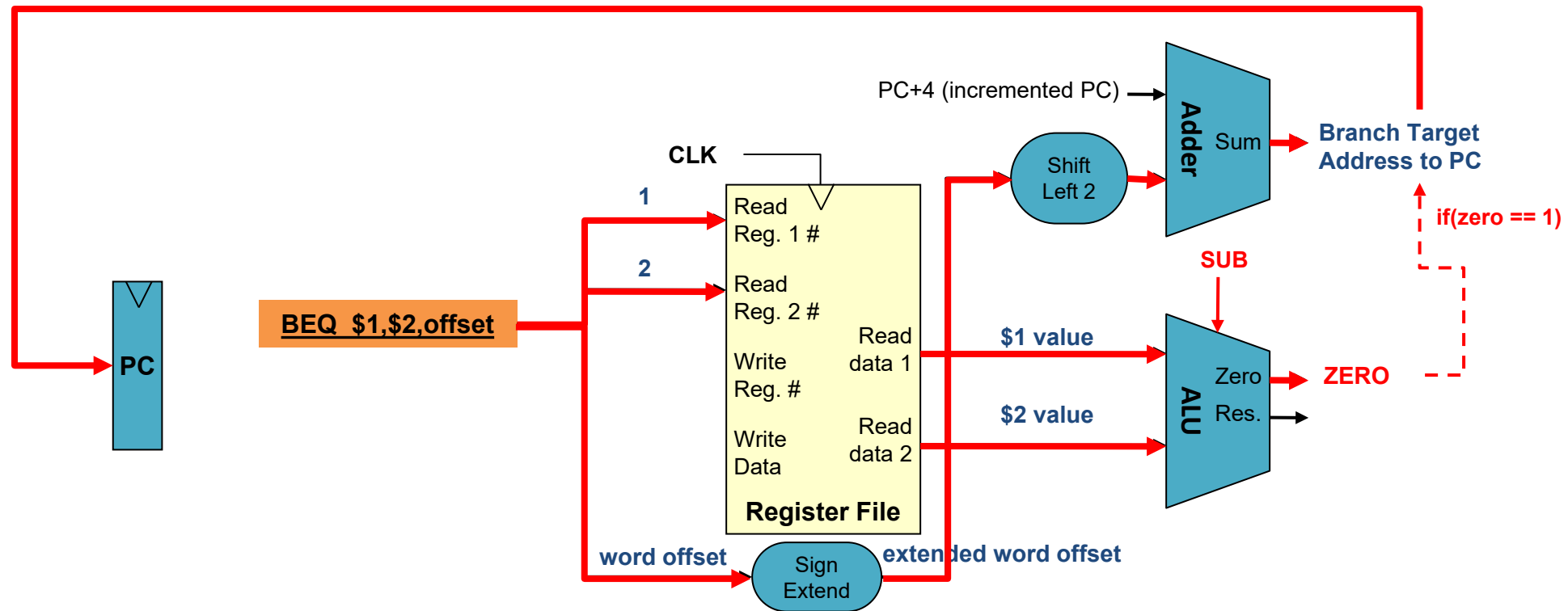- ALU for comparison (examine 'zero' output)
- Sign extension unit for branch offset
- Adder to add PC and offset



Conclusion Time

What are the stages of single-cycle CPU execution?

- Fetch, Decode, Execute, Memory, Writeback

→ IF, ID, EX, MEM, WB

What are the two different ways to calculate addresses in the CPU?

- ALU → Byte addresses, data access.
- Shift-left-2 & Adder → Label, PC.

SAN JOSÉ STATE UNIVERSITY *powering* SILICON VALLEY

